

Experiment # 08: Steady-State AC analysis and Frequency response

Objectives

- Using PSpice to solve steady-state phasor problems
- Observing the frequency response characteristics of different types of analog filters

Part A: Steady-State AC Analysis in PSpice

In addition to DC circuit analysis and transient analysis, PSpice can be used to work steady-state phasor problems.

AC Voltage and Current Sources

The syntax for an AC source is very similar to its DC counterpart. The AC source is assumed to be a *cosine* waveform at a specified phase angle. Its frequency must be defined in a separate " .AC " command that defines the frequency for *all* the sources in the circuit. The unique information for the individual source is: the name, which must start with "V" or "I," the node numbers, the magnitude of the source, and its phase angle. Some examples follow.

*name	nodelist	type	value	phase (deg)	
Vac	4 1	AC	120V	30	
Vba	2 5	AC	240		; phase angle 0 degrees
Ix	3 6	AC	10.0A	-45	; phase angle -45 degrees
Isv	12 9	AC	25mA		; 25 milliamps @ 0 degrees

Here source type, AC, *must* be specified, because the default is DC. If the phase angle is not specified it will be assumed as zero degrees. The units of the phase angle will be in degrees. For voltage source the node on the left is the positive node and the node on the right is the negative node. Similarly, incase of current source positive current flows into the source from the node on the left, passes through the source, and leaves the source from the node on the right.

In some of your previous experiments you have used "SIN" type of source which is one of several useful source types (also EXP, PULSE, PWL, etc) that are used for *transient analysis*. Do not attempt to use SIN for steady-state (phasor) AC analysis nor for frequency sweeps. The SIN type is a time-based function for time-based analysis, whereas the AC type is used in frequency-based modeling. Since phasor analysis uses frequency-based models of circuit elements, always use the AC type as described in this experiment.

Use of the .PRINT AC Command

To enable .PRINT command .AC command must be used. The .AC command was designed to make a sweep of many frequencies for a given circuit. This is called a *frequency response* and will be discussed in Part B of this experiment. Three types of ranges are possible for the frequency sweep: LIN, DEC and OCT. At this time we only want a single frequency to be used so it does not matter which one we choose. We will pick the LIN (linear) range to designate our single frequency.

```

*   type #points  start stop
.AC  LIN   1      60Hz  60Hz;  <== single frequency
.AC  LIN   6      100   200;   <== a linear range sweep
.AC  DEC  20      1Hz   10kHz; <== a logarithmic range sweep

```

The first statement above performs a single analysis using the frequency of 60 Hz. Placing the units "Hz" after the value is optional. The second statement would perform a frequency sweep using frequencies of 100Hz, 120Hz, 140Hz, 160Hz, 180Hz, and 200Hz. The third statement performs a logarithmic range sweep using 20 points per decade over a range of four decades. This will be useful later for studying frequency response of circuits.

Finally, we can discuss the actual .PRINT AC command. Printing the components of phasor values (complex numbers) requires some options. There are four expressions needed for this: magnitude, phase (angle), real part and imaginary part. In addition, we can print voltages or currents. For instance, to print the magnitude of a voltage between nodes 2 and 3, we would specify "VM(2,3)." The phase angle of this same voltage would be "VP(2,3)" and would be printed in degrees. If we need the current magnitude through resistor Rload, we would specify "IM(Rload)." The real part of the voltage on node 7 would be specified "VR(7)" and its imaginary part, "VI(7)." As with the .PRINT DC command, there is no limit on the number of times it can be used in a listing; nor is there a limit on how many print requests can be on a single line.

```

.PRINT AC VM(30,9) VP(30,9); magnitude & angle of voltage
.PRINT AC IR(Rx) II(Rx); real & imag. parts of current through Rx
.PRINT AC VM(17) VP(17) VR(17) VI(17); the whole works on node 17

```

Example Circuit

We will analyze the following circuit at a frequency of 60 Hz.

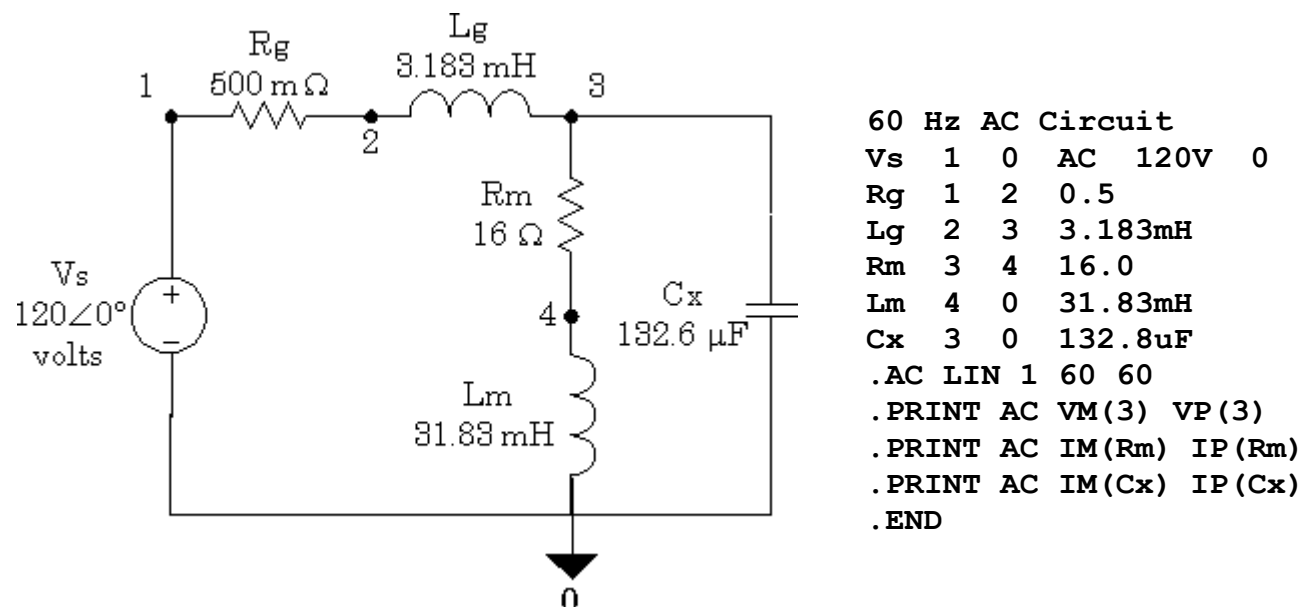


Figure 1

In the above listing, the .AC command sets up the analysis for a single solution at 60 Hz. The .PRINT AC command tells PSpice to report on the voltage magnitude and phase angle at node 3, and the current magnitude and phase angle for the current through resistor Rm and the current magnitude and phase angle through capacitor Cx.

Practice Problem

Draw the circuit shown in figure 1 in schematic and analyze it for the source frequency of 50 Hz. Check whether KCL is satisfied in node 3. Also check KVL for both loops.

Part B: Frequency Sweep

In this section we will discuss frequency sweeps over a range of frequencies. The purpose of this type of analysis is to study the frequency response of different kinds of circuits.

Specifying frequency range for AC Sources

.AC command is used to specify one of the following three types of frequency ranges.

LIN Range Type

The LIN range type is linear. It divides up the range between the minimum and maximum user-specified frequencies into evenly spaced intervals. This is best used to view details over a narrow bandwidth. The first parameter after the keyword LIN is the number of points to calculate. This is followed by the lowest frequency value in Hz, then the highest frequency value in Hz. As with all the range types, the unit "Hz" is optional.

```
.AC LIN 101 2k 4k      ; 101 points from 2 kHz to 4 kHz
.AC LIN 11  800 1000 ; 11  points from 800 Hz to 1 kHz
```

OCT Range Type

The OCT range is logarithmic to the base two. Thus each octave has the same number of points calculated. This is somewhat useful for designing electronic equipment for musical applications. However, the resulting graphs are very similar in appearance to sweeps made with the DEC range. The first parameter after the keyword OCT is the number of points per octave to calculate. This is followed by the lowest frequency value in Hz, then the highest frequency value in Hz.

```
.AC OCT 20 440Hz 1.76kHz; 20 points/octave over 2 octaves
.AC OCT 40 110Hz 880Hz  ; 40 points/octave over 3 octaves
```

DEC Range Type


The DEC range is logarithmic to the base ten. Thus each decade has the same number of points calculated. This is the most commonly used range for making *Bode plots* of a frequency response. The first parameter after the keyword DEC is the number of points per decade to calculate. This is followed by the lowest frequency value in Hz, then the highest frequency value in Hz.

```
.AC DEC 50 1kHz 100kHz ; 50 points/decade over 2 decades
.AC DEC 25 100k 100MEG ; 25 points/decade over 3 decades
```

Probe

The independent variable used by PROBE in a .TRAN analysis is *time*. But in a frequency sweep the independent variable used by PROBE is *frequency*. When PROBE stores data in a transient (.TRAN) analysis, the dependent variables are instantaneous voltages and currents; whereas in a frequency sweep these dependent variables are real and imaginary components of phasor voltages and currents.

Examples of Frequency Sweeps

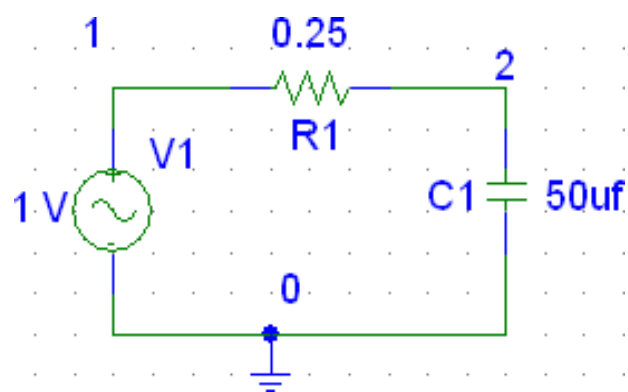


```
First-order low-pass RC filter
Vin 1 0 AC 1.0V
R1 1 2 0.25
C1 2 0 50uF
.AC DEC 20 100Hz 100kHz
.PROBE
.END
```


Figure 2

The above circuit is a first-order low-pass filter. Since we want the gain of this filter, it is convenient to make the input voltage 1 volt so the output voltage is numerically equivalent to the gain. However, the post-processor within PROBE is fully capable of performing arithmetic such as dividing the input voltage into the output voltage.

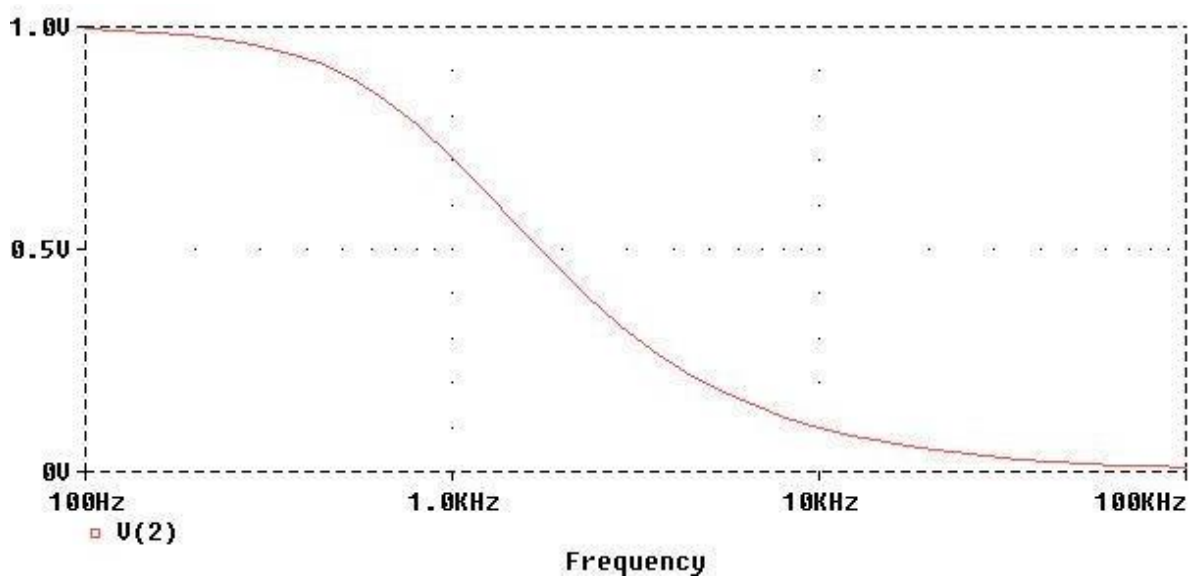
After running this in PSpice, start PROBE, choose "Add" from the "Trace" menu and plot the output voltage. PROBE will provide the following graph.



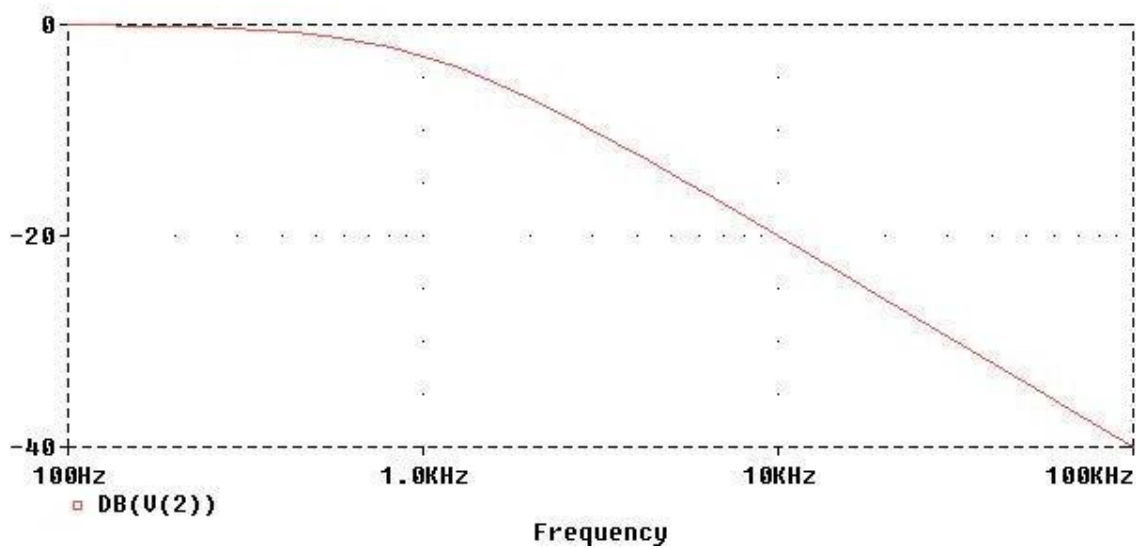Another option is to have PROBE plot the gain in decibels. To do this, choose "Add" from the "Trace" menu in PROBE. Then select the "DB" function in the right-hand column and choose "V(2)" from the left-hand column. After selecting "OK," you should see the following trace.



Notice that the gain is -3db at a frequency of 1 kHz (the half-power frequency) and declines at 20 dB/decade thereafter. The remaining demonstration for this example is to have PROBE plot the *phase shift* of the low-pass filter as a function of frequency. We simply specify "VP(2)" from the "Add Trace" dialog box. Notice that this is the same format used in the .PRINT AC command in PSPICE. PROBE automatically shows the angles in degrees.

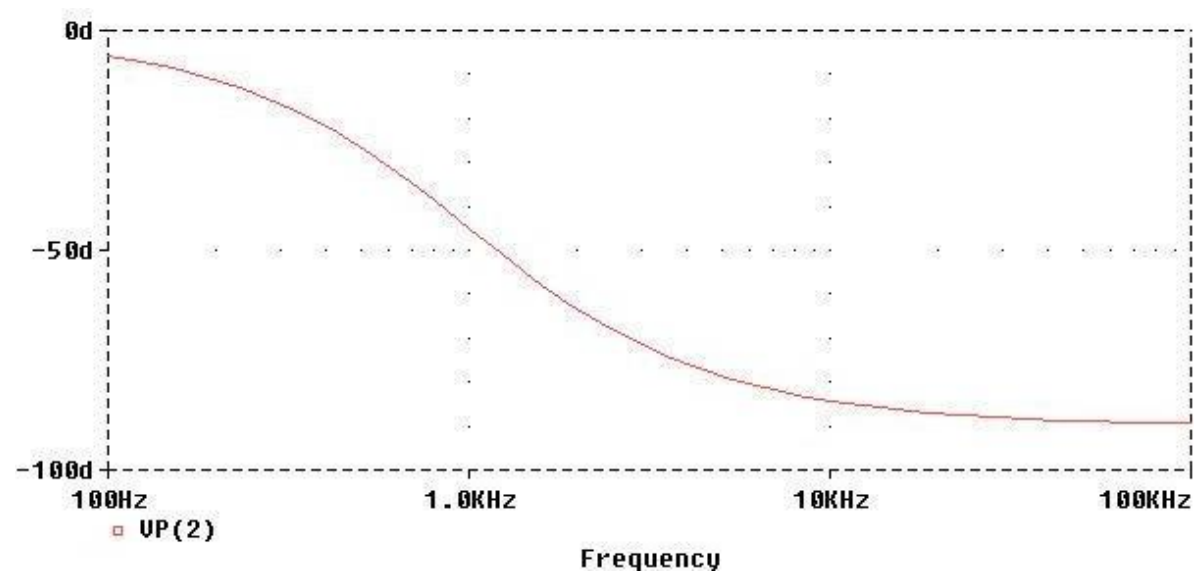

Practice Problem

- (1) Determine the cutoff frequency of the high-pass filter shown in figure 3 by analyzing it using Netlist.

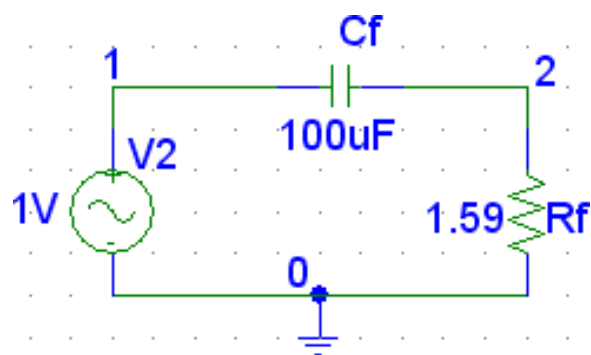


Figure 3

- (2) Cascade the low-pass and high-pass filters shown in figure 2 and figure 3. This arrangement will work as what type of filter? What will the cutoff frequencies?

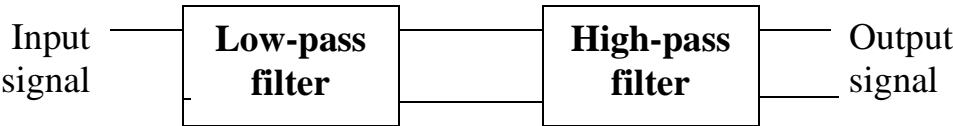


Figure 4

- (3) Examine the following second-order high-pass filter using Schematic. From the output voltage vs frequency plot calculate the cut-off frequency.

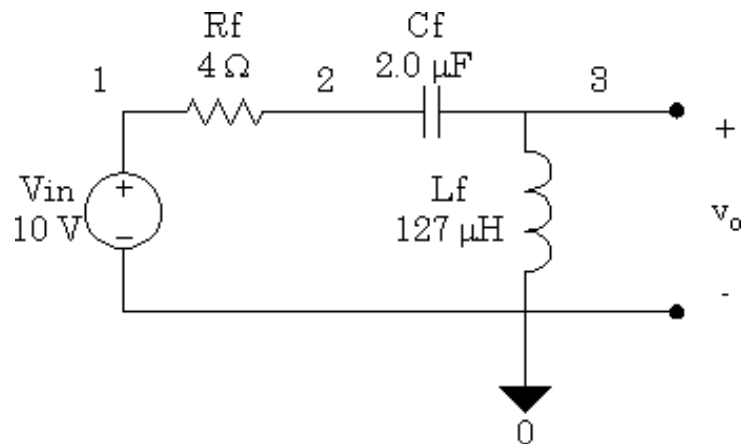


Figure 5

Pre Lab

1. For the circuit shown in figure 1 draw complete phasor diagram and show the magnitudes and phases of all the voltages and currents.
2. For the circuits shown in figure 2 and 3 determine analytical expressions for the magnitudes and phases of $V(2)$ and sketch them quantitatively. Also calculate the $V(2)$ for source signal frequency of 500 Hz, 1 KHz and 15 KHz